




Problems for Chapter 25

1



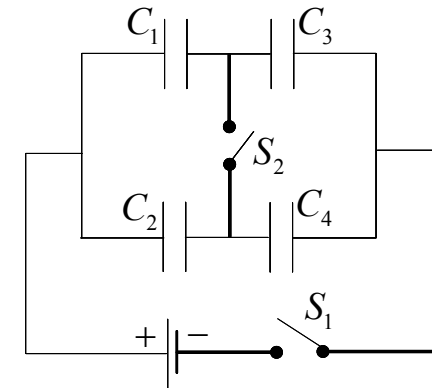Problem: Four capacitors $C_1 = 1.00 \mu F$, $C_2 = 2.00 \mu F$, $C_3 = 4.00 \mu F$, $C_4 = 4.00 \mu F$ and a $12.0 V$ battery are connected as shown in the figure. If only switch 1 is closed, what is the charge on (a) capacitor 1 (b) capacitor 2, (c) capacitor 3, and (d) capacitor 4? If both switches are closed, what is the charge on (e) capacitor 1 (f) capacitor 2, (g) capacitor 3, and (h) capacitor 4?




Solution

In the case when only the switch S_1 is closed, we have the following circuit. It is easy to see that the potential difference applied to the combinations of capacitors C_1 and C_3 (connected in series); and C_2 and C_4 (also connected in series) is the same and equal to V . Due to the fact these capacitors are connected in series they have the same amount of charge on their plates, that is

$$q_1 = q_3, \quad \text{and} \quad q_2 = q_4.$$

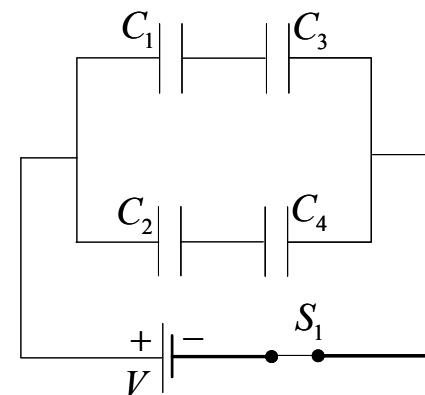The values of charge are given by the formulas





Problems for Chapter 25

2



$$q_1 = q_3 = C_{13}V, \quad \text{and} \quad q_2 = q_4 = C_{24}V,$$

where

$$\frac{1}{C_{13}} = \frac{1}{C_1} + \frac{1}{C_3}, \quad \text{and} \quad \frac{1}{C_{24}} = \frac{1}{C_2} + \frac{1}{C_4}.$$

Using,

$$C_{13} = \frac{C_1 C_3}{C_1 + C_3}, \quad \text{and} \quad C_{24} = \frac{C_2 C_4}{C_2 + C_4},$$

one can get

$$q_1 = q_3 = \frac{C_1 C_3}{C_1 + C_3} V, \quad \text{and} \quad q_2 = q_4 = \frac{C_2 C_4}{C_2 + C_4} V.$$

$$q_1 = q_3 = \frac{(1.00 \mu F)(3.00 \mu F)}{(1.00 \mu F + 3.00 \mu F)} (12.0 V) = \frac{3.00}{4.00} 10^{-6} F (12.0 V) = 9.00 \cdot 10^{-6} F \cdot V = 9.00 \cdot 10^{-6} C,$$

$$q_1 = q_3 = 9.00 \cdot 10^{-6} C.$$



Problems for Chapter 25





3



$$q_2 = q_4 = \frac{(2.00 \mu F)(4.00 \mu F)}{(2.00 \mu F + 4.00 \mu F)}(12.0 V) = \frac{8.00}{6.00} 10^{-6} F (12.0 V) = 16.0 \cdot 10^{-6} F \cdot V,$$

$$q_2 = q_4 = 16.0 \cdot 10^{-6} C.$$

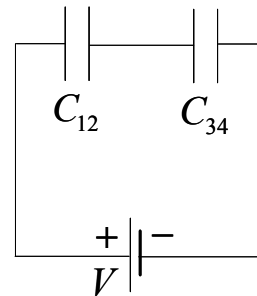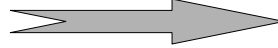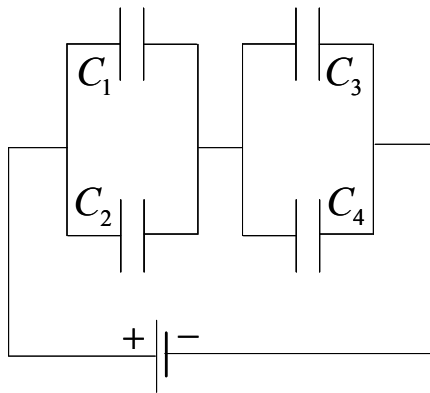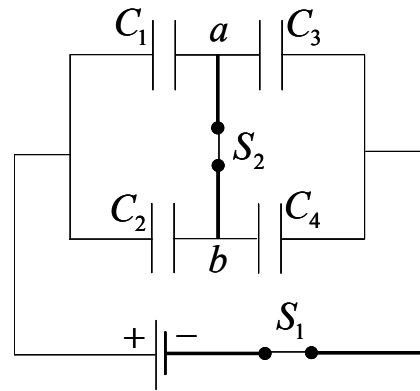In the case when both switches are closed, we have the following circuit, in which the potential difference between the points a and b is zero. Thus, this circuit can be represented as the following equivalent circuit



$$C_{12} = C_1 + C_2,$$

$$C_{34} = C_3 + C_4,$$

$$\frac{1}{C_{tot}} = \frac{1}{C_{12}} + \frac{1}{C_{34}},$$

$$C_{tot} = \frac{C_{12}C_{34}}{C_{12} + C_{34}}.$$





Problems for Chapter 25

4



$$C_{tot} = \frac{(C_1 + C_2)(C_3 + C_4)}{C_1 + C_2 + C_3 + C_4}.$$

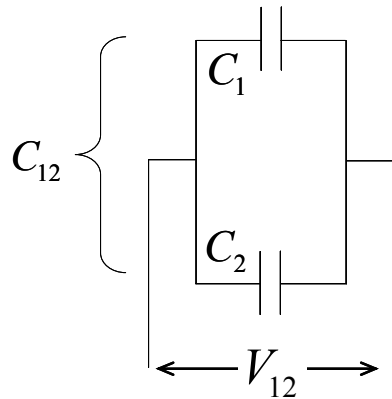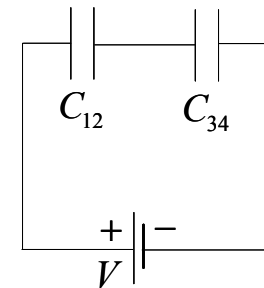Both blocks of capacitors C_{13} and C_{24} have equal charge stored in them




$$q_{12} = q_{34} = C_{tot} V.$$

$$q_{12} = q_1 + q_2, \quad q_{34} = q_3 + q_4$$

$$V_{13} + V_{24} = V.$$
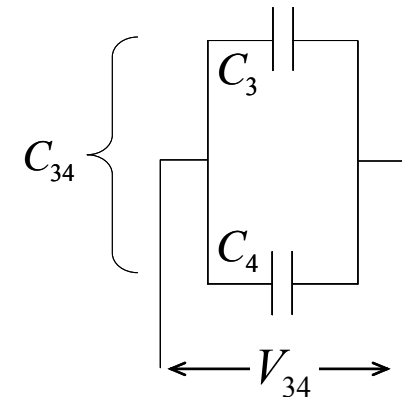
$$V_{12} = \frac{q_{12}}{C_{12}}, \quad V_{34} = \frac{q_{34}}{C_{34}},$$



$$V_{12} = \frac{C_{tot}}{C_{12}} V = \frac{\cancel{(C_1 + C_2)} (C_3 + C_4)}{(C_1 + C_2 + C_3 + C_4) \cancel{(C_1 + C_2)}} V = \frac{(C_3 + C_4)}{(C_1 + C_2 + C_3 + C_4)} V,$$

$$V_{12} = \frac{(C_3 + C_4)}{(C_1 + C_2 + C_3 + C_4)} V.$$



Problems for Chapter 25

5



$$V_{34} = \frac{C_{tot}}{C_{34}} V = \frac{(C_1 + C_2) \cancel{(C_3 + C_4)}}{(C_1 + C_2 + C_3 + C_4) \cancel{(C_3 + C_4)}} V = \frac{(C_1 + C_2)}{(C_1 + C_2 + C_3 + C_4)} V,$$

$$V_{34} = \frac{(C_1 + C_2)}{(C_1 + C_2 + C_3 + C_4)} V.$$

Taking into account that capacitors C_1 and C_3 are connected in parallel, that is the potential difference V_{13} is applied across both capacitors

$$q_1 = V_{12} C_1 = \frac{(C_3 + C_4) C_1}{(C_1 + C_2 + C_3 + C_4)} V, \quad q_2 = V_{12} C_2 = \frac{(C_3 + C_4) C_2}{(C_1 + C_2 + C_3 + C_4)} V,$$

$$q_1 = \frac{(C_3 + C_4) C_1}{(C_1 + C_2 + C_3 + C_4)} V, \quad q_2 = \frac{(C_3 + C_4) C_2}{(C_1 + C_2 + C_3 + C_4)} V.$$

Similar consideration for capacitors C_2 and C_4 gives

$$q_3 = V_{34} C_3 = \frac{(C_1 + C_2) C_3}{(C_1 + C_2 + C_3 + C_4)} V, \quad q_4 = V_{34} C_4 = \frac{(C_1 + C_2) C_4}{(C_1 + C_2 + C_3 + C_4)} V,$$



Problems for Chapter 25

6



$$q_3 = \frac{(C_1 + C_2)C_3}{(C_1 + C_2 + C_3 + C_4)}V, \quad q_4 = \frac{(C_1 + C_2)C_4}{(C_1 + C_2 + C_3 + C_4)}V.$$

$$q_1 = \frac{(3.00\mu F + 4.00\mu F)(1.00\mu F)}{(10.0\mu F)}(12.0V) = \left(\frac{7.00}{10.0} \cdot 10^{-6} F\right)(12.0V) = 8.4 \cdot 10^{-6} C,$$

$$q_1 = 8.4 \cdot 10^{-6} C.$$

$$q_2 = \frac{(7.00\mu F)(2.00\mu F)}{(10.0\mu F)}(12.0V) = \left(\frac{14.0}{10.0} 10^{-6} F\right)(12.0V) = 16.8 \cdot 10^{-6} C,$$

$$q_2 = 16.8 \cdot 10^{-6} C.$$

$$q_3 = \frac{(3.00\mu F)(3.00\mu F)}{(10.0\mu F)}(12.0V) = 10.8 \cdot 10^{-6} C,$$

$$q_3 = 10.8 \cdot 10^{-6} C.$$



Problems for Chapter 25

7





$$q_4 = \frac{(3.00\mu F)(4.00\mu F)}{(10.0\mu F)}(12.0V) = 14.4 \cdot 10^{-6} C,$$

$$q_4 = 14.4 \cdot 10^{-6} C.$$

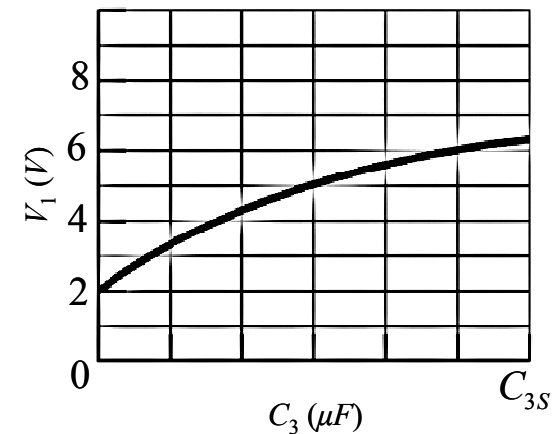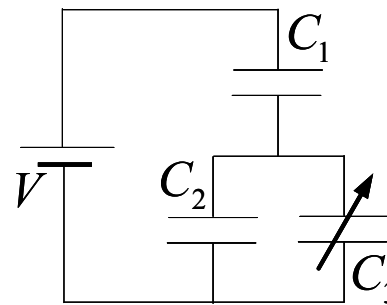Problem: Capacitors C_1 , C_2 , and a variable capacitor C_3 are connected as shown in the figure. The battery supplies a potential difference V to the circuit. The dependence of the potential difference V_1 across the capacitor C_1 as a function of changing capacitance C_3 is presented in the graph.

The horizontal scale in the graph is set by $C_{3S} = 12.0 \mu F$. The potential difference V_1 approaches asymptotic value of $10 V$ as $C_3 \rightarrow \infty$. Find (a) the electric potential across the battery, (b) C_1 , and (c) C_2 .



Solution

The total capacitance of the circuit can be easily found because capacitors C_2 and C_3 are connected in parallel and the block C_{23} is connected in series with C_1 .



Problems for Chapter 25

8



$$\frac{1}{C_{123}} = \frac{1}{C_1} + \frac{1}{C_2 + C_3} = \frac{C_1 + C_2 + C_3}{C_1(C_2 + C_3)}, \quad C_{123} = \frac{C_1(C_2 + C_3)}{(C_1 + C_2 + C_3)}$$

The total charge delivered to the circuit is equal to

$$q = C_{123}V = \frac{C_1(C_2 + C_3)}{(C_1 + C_2 + C_3)}V.$$

By the property of the series connection of capacitors we can conclude that

$$q = q_1 = C_1V_1,$$

thus,

$$V_1 = \frac{q_1}{C_1} = \frac{q}{C_1} = \frac{1}{C_1} \frac{C_1(C_2 + C_3)}{(C_1 + C_2 + C_3)}V, \quad \Rightarrow \quad V_1 = \frac{(C_2 + C_3)}{(C_1 + C_2 + C_3)}V.$$

$$V_1 = \frac{(C_2 + C_3)}{(C_1 + C_2 + C_3)}V.$$



Problems for Chapter 25

9



Let us consider the limit of V_1 when $C_3 \rightarrow \infty$.

$$\lim_{C_3 \rightarrow \infty} V_1 = \lim_{C_3 \rightarrow \infty} \frac{(C_2 + C_3)}{(C_1 + C_2 + C_3)} V = V \lim_{C_3 \rightarrow \infty} \frac{\cancel{C_3} (1 + C_2 / C_3)}{\cancel{C_3} [1 + (C_1 + C_2) / C_3]} = V,$$


Using the $V_1 = 10 \text{ V}$ when $C_3 \rightarrow \infty$, we have that the potential difference across the battery is

$$V = 10 \text{ V}.$$

Let us consider the dependence of V_1 on C_3

$$V_1 = \frac{(C_2 + C_3)}{(C_1 + C_2 + C_3)} V.$$

When $C_3 = 0$, $V_1 = 2V$

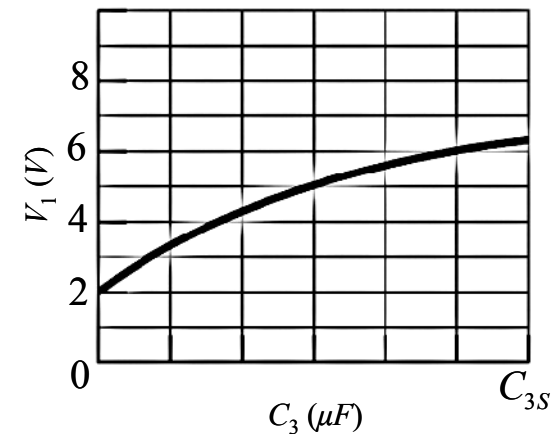

$$2V = \frac{(C_2 + 0)}{(C_1 + C_2 + 0)} (10V), \quad \Rightarrow \quad 1 = \frac{C_2}{(C_1 + C_2)} 5, \quad \Rightarrow \quad (C_1 + C_2) = 5C_2,$$



Problems for Chapter 25

10



$$C_1 + C_2 = 5C_2, \quad \Rightarrow \quad C_1 = 4C_2,$$

As the graph shows at $C_3 = 6.0 \mu F$, V_1 is exactly half of the battery voltage. Thus,


$$V_1 = \frac{(C_2 + C_3)}{(C_1 + C_2 + C_3)} V, \quad \Rightarrow$$

$$5V = \frac{(C_2 + 6.0 \mu F)}{(4C_2 + C_2 + 6.0 \mu F)} (10V),$$

$$1 = \frac{(C_2 + 6.0 \mu F)}{(5C_2 + 6.0 \mu F)} 2, \quad \Rightarrow \quad (5C_2 + 6.0 \mu F) = 2(C_2 + 6.0 \mu F),$$

$$5C_2 + 6.0 \mu F = 2C_2 + 12.0 \mu F, \quad \Rightarrow \quad 3C_2 = 6.0 \mu F, \quad C_2 = 3.0 \mu F.$$

$$C_1 = 12.0 \mu F.$$

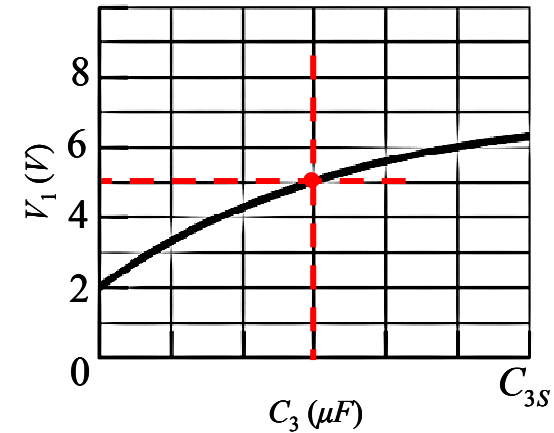




Problems for Chapter 25

11






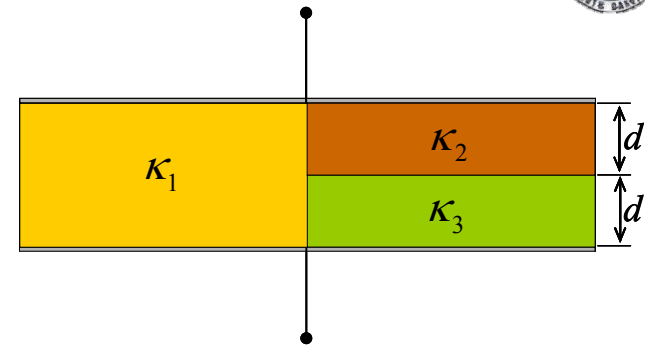Problem: A parallel plate capacitor has the plate area $A = 10.5 \text{ cm}^2$ and plate separation $2d = 7.12 \text{ mm}$. Half of this capacitor is filled with dielectric material with dielectric constant $\kappa_1 = 21.0$ and another half is filled with two different dielectrics (see figure) with $\kappa_2 = 42.0$ and $\kappa_3 = 58.0$. Find the capacitance of the capacitor.



Solution

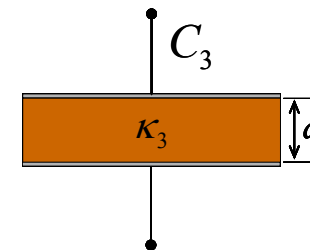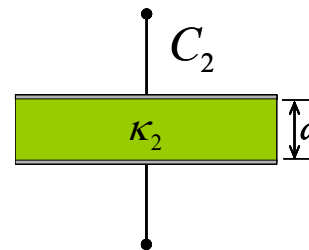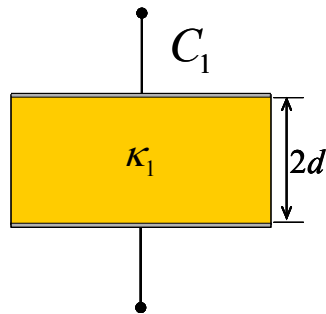Let us consider this capacitor as a combination of three capacitors and figure out the type of their connections. The plate area of each capacitor is equal to $A/2$.



Capacitances of these capacitors are $C_1 = \kappa_1 \frac{\epsilon_0 A}{4d}$, $C_2 = \kappa_2 \frac{\epsilon_0 A}{2d}$, $C_3 = \kappa_3 \frac{\epsilon_0 A}{2d}$.




Problems for Chapter 25

12



The capacitors are connected as follows

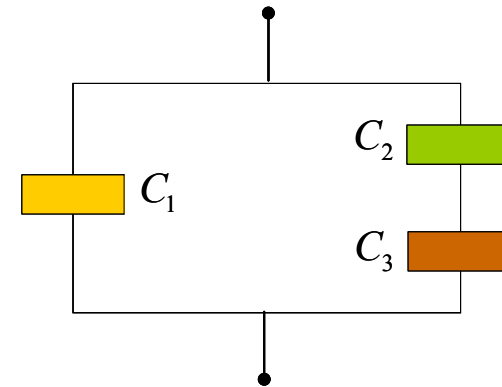

$$C = C_1 + C_{23}, \quad C_{23} = \frac{C_2 C_3}{(C_2 + C_3)},$$

$$C = C_1 + \frac{C_2 C_3}{(C_2 + C_3)} = \frac{C_1(C_2 + C_3) + C_2 C_3}{(C_2 + C_3)} = \frac{C_1 C_2 + C_1 C_3 + C_2 C_3}{(C_2 + C_3)}, \quad C = \frac{C_1 C_2 + C_1 C_3 + C_2 C_3}{(C_2 + C_3)}.$$

$$C = \frac{\frac{\kappa_1 \varepsilon_0 A}{4d} \frac{\kappa_2 \varepsilon_0 A}{2d} + \frac{\kappa_1 \varepsilon_0 A}{4d} \frac{\kappa_3 \varepsilon_0 A}{2d} + \frac{\kappa_2 \varepsilon_0 A}{2d} \frac{\kappa_3 \varepsilon_0 A}{2d}}{\frac{\kappa_2 \varepsilon_0 A}{2d} + \frac{\kappa_3 \varepsilon_0 A}{2d}} = \frac{(\varepsilon_0 A)^2 \left[\frac{\kappa_1 \kappa_2}{2} + \frac{\kappa_1 \kappa_3}{2} + \kappa_2 \kappa_3 \right]}{\frac{\varepsilon_0 A}{2d} (\kappa_2 + \kappa_3)}$$

$$= \frac{\varepsilon_0 A \left[\frac{\kappa_1 \kappa_2}{2} + \frac{\kappa_1 \kappa_3}{2} + \kappa_2 \kappa_3 \right]}{2d (\kappa_2 + \kappa_3)} = \frac{\varepsilon_0 A \left[\kappa_1 \kappa_2 + \kappa_1 \kappa_3 + 2\kappa_2 \kappa_3 \right]}{2d \cdot 2(\kappa_2 + \kappa_3)}, \quad C = \frac{\varepsilon_0 A (\kappa_1 \kappa_2 + \kappa_1 \kappa_3 + 2\kappa_2 \kappa_3)}{4d (\kappa_2 + \kappa_3)}.$$




$$C = \frac{(8.85 \cdot 10^{-12} \text{ C}^2 / \text{N} \cdot \text{m}^2)(1.05 \cdot 10^3 \text{ m}^2)(21.0) \cdot (42.0) + (21.0) \cdot (58.0) + 2(42.0) \cdot (58.0)}{4(3.56 \cdot 10^3 \text{ m})(42.0) + (58.0)}$$

$$= \frac{8.85 \cdot 1.05}{4 \cdot 3.56} 10^{-12} \left(\frac{\text{C}^2}{\text{N} \cdot \text{m}} \right) \frac{882 + 1218 + 4872}{100} = 0.653 \cdot 10^{-14} \left(\frac{\text{C}^2}{\text{J}} \right) (882 + 1218 + 4872)$$

$$= 0.653 \cdot 10^{-14} \left(\frac{\text{C}}{\text{V}} \right) 6.972 \cdot 10^3 = 4.55 \cdot 10^{-11} \text{ F},$$

$$C = 4.55 \cdot 10^{-11} \text{ F}.$$

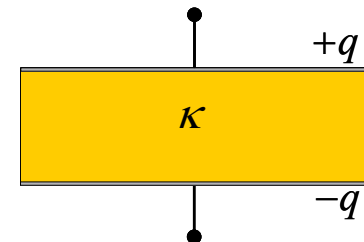Problem: Two parallel plates of area 100 cm^2 are charged with equal magnitudes $q = 8.9 \cdot 10^{-7} \text{ C}$ but opposite signs of charge. The electric field within the dielectric material filling the space between plates is $1.4 \cdot 10^6 \text{ V/m}$. Calculate (a) the dielectric constant of material, (b) the magnitude of the charge induced on the surfaces of dielectric.



Solution

(a) The dielectric constant of material is determined by $\kappa = E_0 / E,$



Problems for Chapter 25

14



where E_0 is the field in vacuum and E is the field in dielectric. To find the field in vacuum one can use the formula

$$E = \frac{\sigma}{\epsilon_0}, \quad \text{where} \quad \sigma = q / A.$$

Thus,

$$\kappa = \frac{\sigma}{\epsilon_0 E} = \frac{q}{\epsilon_0 A E}.$$

$$\begin{aligned} \kappa &= \frac{(8.9 \cdot 10^{-7} \text{ C})}{(8.85 \cdot 10^{-12} \text{ C}^2 / \text{N} \cdot \text{m}^2)(10^{-2} \text{ m}^2)(1.4 \cdot 10^6 \text{ V} / \text{m})} \\ &= \frac{8.9}{8.85 \cdot 1.4} \frac{10^{-7}}{10^{-12} \cdot 10^{-2} \cdot 10^6} \frac{\text{C} \cdot \text{N} \cdot \cancel{\text{m}^2} \cdot \text{m}}{\text{C}^2 \cdot \text{V} \cdot \cancel{\text{m}^2}} = 0.72 \cdot 10 \frac{\text{J}}{\text{C} \cdot \text{V}} = 7.2 \frac{\text{J} \cdot \text{C}}{\text{C} \cdot \text{J}} = 7.2, \end{aligned}$$

$$\kappa = 7.2.$$



Problems for Chapter 25

15



The charge induced on the surface of dielectric is equal to

$$q' = q \left(1 - \frac{1}{\kappa} \right).$$

$$q' = (8.9 \cdot 10^{-7} \text{ C}) \left(1 - \frac{1}{7.2} \right) = 7.7 \cdot 10^{-7} \text{ C},$$

$$q' = 7.7 \cdot 10^{-7} \text{ C}.$$