

Name SOLUTION

EE301 Dec. 4, 2009

Quiz 10 - No Calculators - pencil (or pen) and paper only


Problem 1:

If $v_s(t) = 4\sin(t)$, find $v_o(t)$ and plot both waveforms. Assume the diode is ideal.


$$\omega = 1$$

$$f = \frac{\omega}{2\pi} = \frac{1}{2\pi} \text{ Hz}$$


$$T = 2\pi \text{ sec/cyc}$$

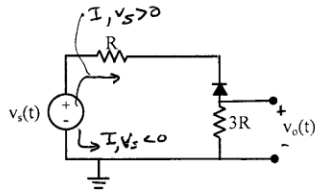

FOR $V_s > 0$
REVERSE BIASED
 $I_D = 0$

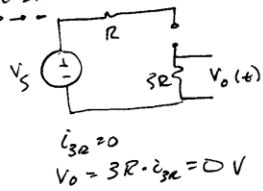


FOR $V_s < 0$
FORWARD BIASED
 $I_D = I$

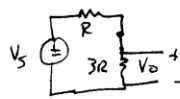

$$v_o = \frac{3R}{3R+R} \cdot v_s$$


$$= \frac{3R}{4R} \cdot v_s = \frac{3}{4} v_s$$
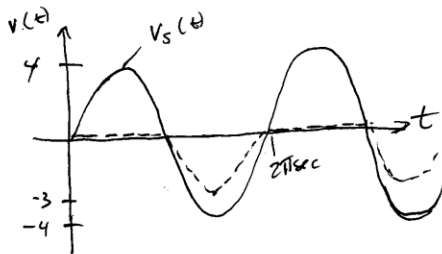
$$v_o = \frac{3}{4} (4\sin(t)) = \underline{\underline{3\sin(t) = v_o(t)}}$$



Problem 2 on back side

Problem 2

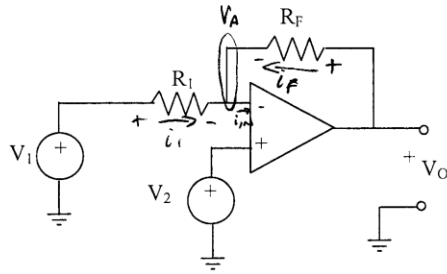

Find V_0 in terms of the resistors and sources assuming an **ideal** op-amp. Hint: Use KCL

FOR AN IDEAL OP AMP $\rightarrow \begin{cases} i_{IN} = 0 \\ V^+ = V^- \end{cases}$

$$V^+ = V_2$$

$$V_A = V^- = V^+ = V_2$$

KCL @ A

$$i_1 + i_F - i_{IN} = 0$$

$$\left[\frac{V_1 - V_A}{R_1} \right] + \left[\frac{V_0 - V_A}{R_F} \right] = 0$$

$$\frac{V_0}{R_F} = -\left[\frac{1}{R_1} \right] V_1 + \left[\frac{1}{R_1} + \frac{1}{R_F} \right] V_A$$

$$V_0 = \left[-\frac{R_F}{R_1} \right] V_1 + \left[\frac{R_F}{R_1} + 1 \right] V_2$$