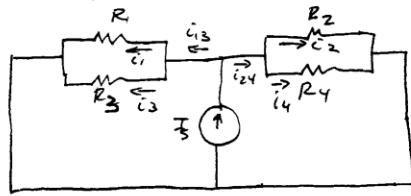


PROBLEM!



GIVEN: $R_1 = 10\Omega$, $R_2 = 15\Omega$, $R_3 = 10\Omega$
 $R_4 = 30\Omega$, $I_s = 12A$


- FIND:
- R_{eq}
 - i_{R1} , i_{R2} , i_{R3} , i_{R4}
 - V_{R1} , V_{R2} , V_{R3} , V_{R4}
 - V_{I_s}

$$R_{13} = R_1 \parallel R_3 = \frac{1}{\frac{1}{R_1} + \frac{1}{R_3}} = \frac{1}{\frac{1}{10} + \frac{1}{10}} =$$


$$R_{13} = 5\Omega$$

$$R_{24} = R_2 \parallel R_4 = \frac{1}{\frac{1}{R_2} + \frac{1}{R_4}} = \frac{1}{\frac{1}{15} + \frac{1}{30}} =$$

$$R_{24} = 10\Omega$$

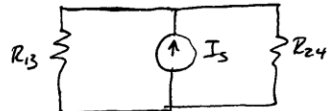

CAN ALSO BE DRAWN

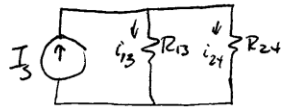

$$R_{eq} = R_{13} \parallel R_{24} = \frac{1}{\frac{1}{R_{13}} + \frac{1}{R_{24}}} = \frac{1}{\frac{1}{5} + \frac{1}{10}} = 3.33\Omega$$

$$R_{eq} = 3.33\Omega \leftarrow$$

SOURCE CURRENT SPLITS BETWEEN R_{13} & R_{24}

$$i_{13} = \frac{\frac{1}{R_{13}}}{\frac{1}{R_{13}} + \frac{1}{R_{24}}} \cdot I_s = \frac{\frac{1}{5}}{\frac{1}{5} + \frac{1}{10}} \cdot 12$$

$$i_{13} = 8A$$

$$i_{24} = \frac{\frac{1}{R_{24}}}{\frac{1}{R_{13}} + \frac{1}{R_{24}}} \cdot I_s = \frac{\frac{1}{10}}{\frac{1}{5} + \frac{1}{10}} \cdot 12$$

$$i_{24} = 4A$$

i_{R13} SPLITS BETWEEN R_1 & R_3

$$i_{R1} = \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_3}} \cdot i_{R13} = \frac{\frac{1}{10}}{\frac{1}{10} + \frac{1}{10}} \cdot 8$$

$$i_{R1} = 4A \leftarrow$$

$$i_{R3} = \frac{\frac{1}{R_3}}{\frac{1}{R_1} + \frac{1}{R_3}} \cdot i_{R13} = \frac{\frac{1}{10}}{\frac{1}{10} + \frac{1}{10}} \cdot 8$$

$$i_{R3} = 4A \leftarrow$$

i_{R24} SPLITS BETWEEN R_2 & R_4

$$i_{R2} = \frac{\frac{1}{R_2}}{\frac{1}{R_2} + \frac{1}{R_4}} \cdot i_{R24} = \frac{\frac{1}{15}}{\frac{1}{15} + \frac{1}{30}} \cdot 4$$

$$i_{R2} = 2.66A \leftarrow$$

$$i_{R4} = \frac{\frac{1}{R_4}}{\frac{1}{R_2} + \frac{1}{R_4}} \cdot i_{R24} = \frac{\frac{1}{30}}{\frac{1}{15} + \frac{1}{30}} \cdot 4$$


$$i_{R4} = 1.33A \leftarrow$$

ALL RESISTORS & SOURCE SHARE THE SAME 2 NODES & THEREFORE ARE IN PARALLEL

$$V_{I_s} = V_{R1} = V_{R2} = V_{R3} = V_{R4} = R_{eq} \cdot I_s = (3.33)(12) = 40V$$

$V_{I_s} = 40V$
$V_{R1} = 40V$
$V_{R2} = 40V$
$V_{R3} = 40V$
$V_{R4} = 40V$

PROBLEM 2

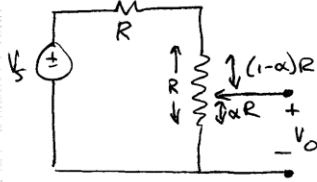

Given: Circuit Diagram

Find: • THE CURRENT THROUGH EACH ELEMENT IN TERMS OF R, α, V_s

• V_o AS A FUNCTION OF α & V_s

• PLOT V_o AS A FUNCTION OF α AS α VARIES FROM $0 \rightarrow 1$.

$$R_{eq} = R + R = 2R$$

$$i = \frac{V_s}{R_{eq}} = \frac{V_s}{2R}$$

$$i = \frac{V_s}{2R} \quad \leftarrow \text{NOTE SERIES CIRCUIT SO ALL CURRENTS ARE THE SAME}$$

$$V_o = \alpha R \cdot i$$

$$= \alpha R \cdot \frac{V_s}{2R}$$

$$V_o = \frac{\alpha}{2} \cdot V_s$$

OR USING VOLTAGE DIVISION


$$V_o = \frac{\alpha R}{R + R} \cdot V_s$$

$$V_o = \frac{\alpha R}{2R} \cdot V_s$$

$$V_o = \frac{\alpha}{2} \cdot V_s$$

$$\text{IF } \alpha = 0 \Rightarrow V_o = 0$$

$$\text{IF } \alpha = 1 \Rightarrow V_o = \frac{1}{2} V_s$$

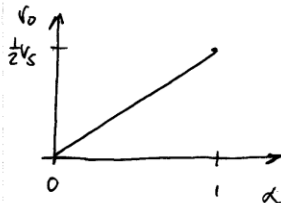

PROBLEM 3

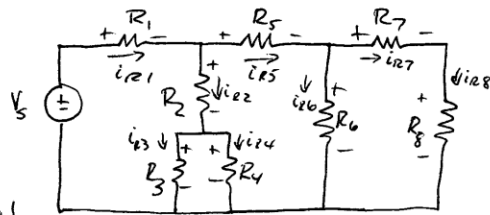


Fig 1

$$R_{78} = R_7 + R_8 = 50 + 30 = 80$$

$$R_{78} = 80 \Omega \leftarrow$$

$$R_{34} = R_3 \parallel R_4 = \frac{1}{\frac{1}{60} + \frac{1}{40}} = 15$$

$$R_{34} = 15 \Omega \leftarrow$$

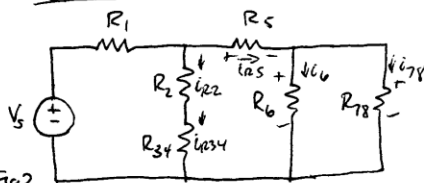


Fig 2

$$R_{678} = R_6 \parallel R_{78} = \frac{1}{\frac{1}{R_6} + \frac{1}{R_{78}}} = \frac{1}{\frac{1}{20} + \frac{1}{80}}$$

$$R_{678} = 16 \Omega \leftarrow$$

$$R_{234} = R_2 + R_{34} = 25 + 15 = 40$$

$$R_{234} = 40 \Omega \leftarrow$$

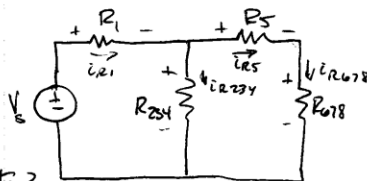


Fig 3

$$R_{5 \rightarrow 8} = R_5 + R_{678} = 24 + 16$$

$$R_{5 \rightarrow 8} = 40 \Omega \leftarrow$$

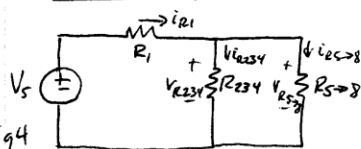


Fig 4

$$R_{2 \rightarrow 8} = R_{234} \parallel R_{5 \rightarrow 8} = \frac{1}{\frac{1}{R_{234}} + \frac{1}{R_{5 \rightarrow 8}}} = \frac{1}{\frac{1}{40} + \frac{1}{40}}$$

$$R_{2 \rightarrow 8} = 20 \Omega \leftarrow$$

Given: $R_1 = 10 \Omega, R_2 = 25 \Omega, R_3 = 60 \Omega$
 $R_4 = 20 \Omega, R_5 = 24 \Omega, R_6 = 20 \Omega$
 $R_7 = 50 \Omega, R_8 = 30 \Omega, V_s = 15V$

FIND: - VOLTAGE ACROSS EACH RESISTOR

- CURRENT THROUGH EACH RESISTOR

- CURRENT SUPPLIED BY SOURCE

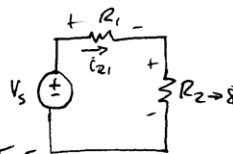


Fig 5

$$R_{eq} = R_1 + R_2 \rightarrow 8 = 10 + 20 = 30$$

$$R_{eq} = 30 \Omega \leftarrow$$



Fig 6

$$i_{Vs} = \frac{V_s}{R_{eq}} = \frac{15}{30}$$

$$i_{Vs} = 0.5A \leftarrow$$

FROM FIG 5

$$V_{R1} = \frac{R_1}{R_1 + R_2 \rightarrow 8} \cdot V_s = \frac{10}{10 + 20} \cdot 15$$

$$V_{R1} = 5V \leftarrow$$

$$V_{R2 \rightarrow 8} = \frac{R_2 \rightarrow 8}{R_1 + R_2 \rightarrow 8} \cdot V_s = \frac{20}{10 + 20} \cdot 15$$

$$V_{R2 \rightarrow 8} = 10V \leftarrow$$

$$i_{R1} = i_{Vs} \rightarrow i_{R1} = 0.5A \leftarrow$$

$$i_{R2 \rightarrow 8} = i_{Vs} \rightarrow i_{R2 \rightarrow 8} = 0.5A \leftarrow$$

PROBLEM 3 CONT.

FROM FIG. 4

$$V_{R234} = V_{R5 \rightarrow 8} = V_{R2 \rightarrow 8} = 10V$$

$$i_{R234} = \frac{\frac{1}{R_{234}}}{\frac{1}{R_{234}} + \frac{1}{R_{5 \rightarrow 8}}} \cdot i_{R1}$$

$$= \frac{\frac{1}{40}}{\frac{1}{40} + \frac{1}{40}} \cdot 0.5$$

$$i_{R234} = 0.25A \leftarrow$$

$$i_{R5 \rightarrow 8} = \frac{\frac{1}{R_{5 \rightarrow 8}}}{\frac{1}{R_{234}} + \frac{1}{R_{5 \rightarrow 8}}} \cdot i_{R1}$$

$$= \frac{\frac{1}{40}}{\frac{1}{40} + \frac{1}{40}} \cdot 0.5$$

$$i_{R5 \rightarrow 8} = 0.25A \leftarrow$$

FROM FIG. 3

$$i_{R5} = i_{R678} = i_{R5 \rightarrow 8} = 0.25A$$

$$i_{R5} = 0.25A \leftarrow$$

$$i_{R678} = 0.25A \leftarrow$$

$$V_{R5} = \frac{R_5}{R_5 + R_{678}} \cdot V_{R5678}$$

$$V_{R5} = \frac{24}{24 + 16} \cdot 10V$$

$$V_{R5} = 6V \leftarrow$$

$$V_{R678} = \frac{R_{678}}{R_5 + R_{678}} \cdot V_{R5678}$$

$$V_{R678} = \frac{16}{24 + 16} \cdot 10$$

$$V_{R678} = 4V \leftarrow$$

FROM FIG. 2

$$i_{R2} = i_{R34} = i_{R234} = 0.25A$$

$$i_{R2} = 0.25A \leftarrow$$

$$i_{R34} = 0.25A \leftarrow$$

$$V_{R2} = \frac{R_2}{R_2 + R_{34}} \cdot V_{R234}$$

$$V_{R2} = \frac{25}{25 + 15} \cdot 10$$

$$V_{R2} = 6.25V \leftarrow$$

$$V_{R34} = \frac{15}{25 + 15} \cdot 10$$

$$V_{R34} = 3.75V \leftarrow$$

$$V_{R6} = V_{R78} = V_{R678} = 4V$$

$$V_{R6} = 4V \leftarrow$$

$$V_{R678} = 4V \leftarrow$$

$$i_{R6} = \frac{\frac{1}{R_6}}{\frac{1}{R_6} + \frac{1}{R_{78}}} \cdot i_{R5} = \frac{\frac{1}{20}}{\frac{1}{20} + \frac{1}{80}} \cdot 0.25$$

$$i_{R6} = 0.2A \leftarrow$$

$$i_{R78} = \frac{\frac{1}{R_{78}}}{\frac{1}{R_6} + \frac{1}{R_{78}}} \cdot i_{R5} = \frac{\frac{1}{80}}{\frac{1}{20} + \frac{1}{80}} \cdot 0.25$$

$$i_{R78} = 0.05A \leftarrow$$

PROBLEM 3 CONT.

FROM FIGURE 1

$$i_{R7} = i_{R8} = i_{R78}$$

$$\boxed{i_{R7} = 0.05 \text{ A}} \leftarrow$$

$$\boxed{i_{R8} = 0.05 \text{ A}} \leftarrow$$

$$V_{R7} = \frac{R_7}{R_7 + R_8} \cdot V_{R78}$$

$$= \frac{50}{50 + 30} \cdot 4$$

$$\boxed{V_{R7} = 2.5 \text{ V}} \leftarrow$$

$$V_{R8} = \frac{R_8}{R_7 + R_8} \cdot V_{R78}$$

$$= \frac{30}{50 + 30} \cdot 4$$

$$\boxed{V_{R8} = 1.5 \text{ V}} \leftarrow$$

$$V_{R3} = V_{R4} = V_{R34}$$

$$\boxed{V_{R3} = 3.75 \text{ V}} \leftarrow$$

$$\boxed{V_{R4} = 3.75 \text{ V}} \leftarrow$$

$$i_{R3} = \frac{\frac{1}{R_3}}{\frac{1}{R_3} + \frac{1}{R_4}} \cdot i_{R34}$$

$$i_{R3} = \frac{\frac{1}{60}}{\frac{1}{60} + \frac{1}{30}} \cdot 0.25$$



$$\boxed{i_{R3} = 0.0625 \text{ A}} \leftarrow$$

$$i_{R4} = \frac{\frac{1}{R_4}}{\frac{1}{R_3} + \frac{1}{R_4}} \cdot i_{R34}$$

$$= \frac{\frac{1}{20}}{\frac{1}{60} + \frac{1}{20}} \cdot 0.25$$

$$\boxed{i_{R4} = 0.1875 \text{ A}} \leftarrow$$

PROBLEM 4

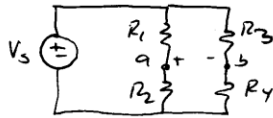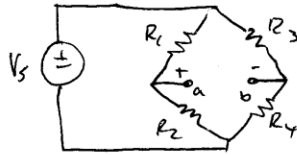

Given: $V_s = 12V$, $R_1 = 220\Omega$, $R_2 = 220\Omega$
 $R_3 = 220\Omega$, $R_4 = 220.05\Omega$

FIND: THE VOLTAGE BETWEEN NODES a & b, V_{ab}

$$V_a = V_{R2} = \frac{R_2}{R_1 + R_2} \cdot V_s = \frac{220}{220 + 220} \cdot 12V$$

$$V_a = 6V$$

$$V_b = V_{R4} = \frac{R_4}{R_3 + R_4} \cdot V_s = \frac{220.05}{220 + 220.05} \cdot 12V$$

$$V_b = 6.00068V$$


$$V_{ab} = V_a - V_b = (6 - 6.00068)V$$

$$V_{ab} = -0.00068V$$

$$V_{ab} = -0.68mV$$

PROBLEM 5


Part a)

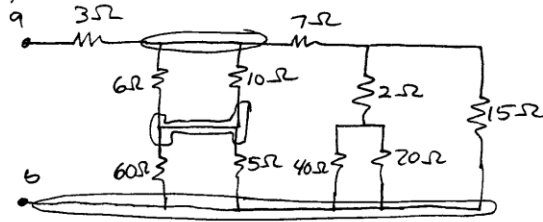

$$20\Omega // 40\Omega = \frac{1}{\frac{1}{20} + \frac{1}{40}} = 13\frac{1}{3}\Omega$$


$$6\Omega // 10\Omega = \frac{1}{\frac{1}{6} + \frac{1}{10}} = 3.75\Omega$$
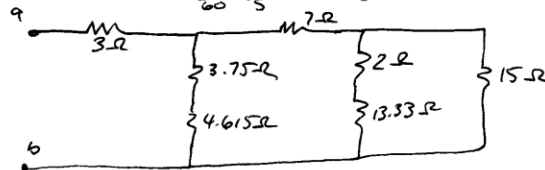
$$60\Omega // 15\Omega = \frac{1}{\frac{1}{60} + \frac{1}{15}} = 4.615\Omega$$




$$3.75 + 4.615 = 8.365$$


$$2 + 13.33 = 15.33$$

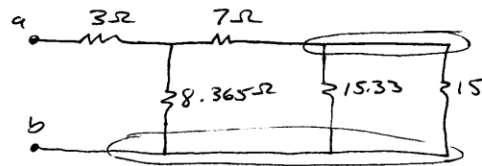

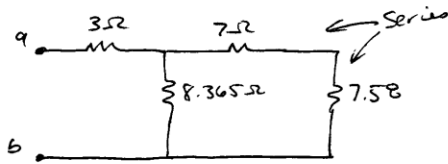
$$15 // 15.33 = \frac{1}{\frac{1}{15} + \frac{1}{15.33}} = 7.58\Omega$$



$$7 + 7.58 = 14.58\Omega$$

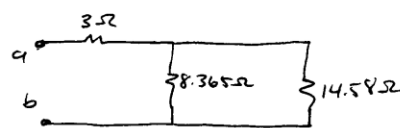
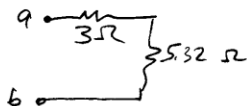
$$8.365 // 14.58 = \frac{1}{\frac{1}{8.365} + \frac{1}{14.58}} = 5.32\Omega$$






$$R_{ab} = 3 + 5.32$$


$$\underline{R_{ab} = 8.32\Omega}$$

PROBLEM 5 CONT.


PART b

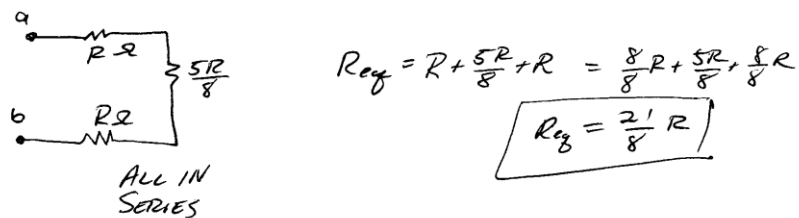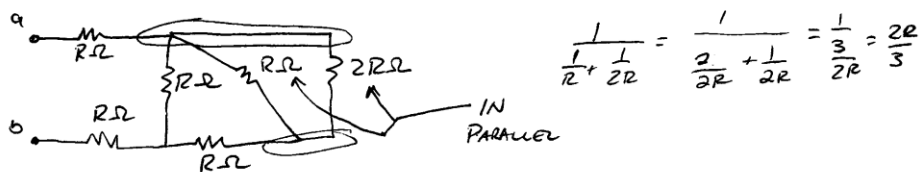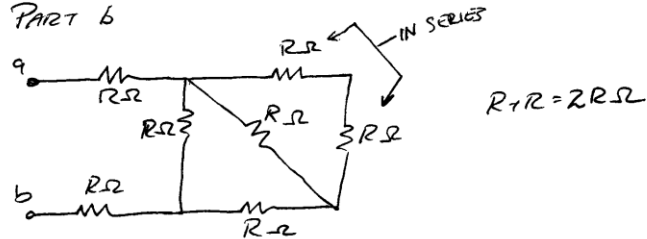

PROBLEMS
PART C

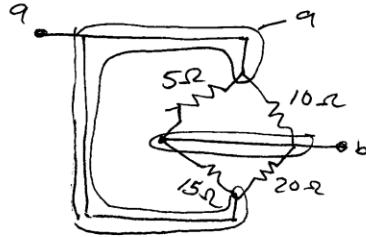

WILL HAVE TO REDRAW

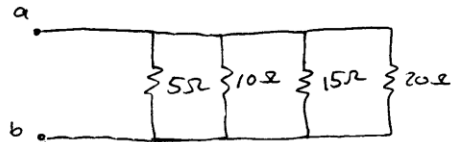


$$R_{ab} = \frac{1}{\frac{1}{5} + \frac{1}{10} + \frac{1}{15} + \frac{1}{20}} = \underline{\underline{2.4 \Omega}} = R_{ab} \leftarrow$$

$$= \frac{12 \Omega}{5} = R_{ab} \leftarrow \text{OR}$$





PROBLEM 5

Part d.

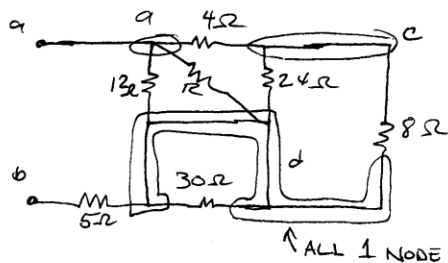

FIND R SUCH THAT THE EQUIVALENT RESISTANCE BETWEEN a & b IS 9Ω

MAY HELP TO REDRAW

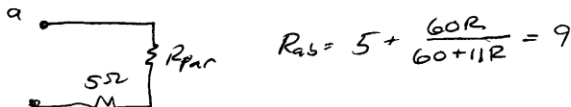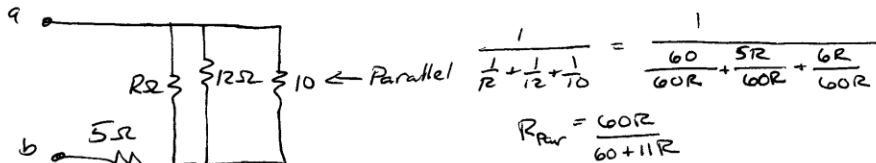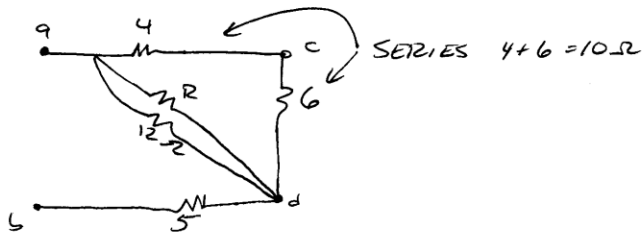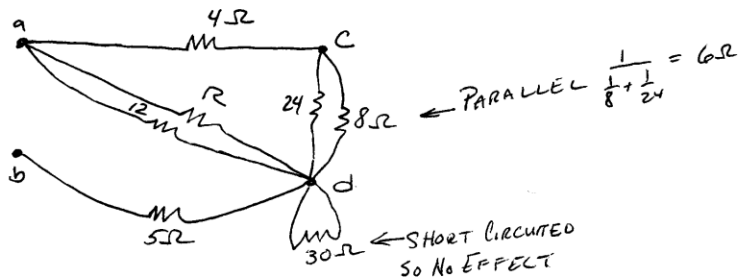

PROBLEMS part 4 cont.

$$R_{ab} = 5 + \frac{60R}{60+11R} = 9$$

$$\frac{60R}{60+11R} = 4$$

$$60R = 4(60+11R)$$

$$60R = 240 + 44R$$

$$16R = 240$$

$$R = \frac{240}{16}$$

$$\underline{R = 15\Omega} \leftarrow$$